

Course Title: Electronic Circuits (2)  
Date: 28/05/2016Course Code: EEC 2206  
Allowed time: 3 HoursYear: **second year**  
No. of Pages: (4)**Remarks:** (answer the following questions... assume any missing data... arrange your answer booklet)

Use graphs and examples whenever you have a chance during your answer

**Question No. 1 : (18) Marks**A. Determine  $Z_i$ ,  $Z_o$ ,  $A_v$  and  $V_o$  for the network of **Fig.1** if  $V_i = 0.1$  mV. **(6) Marks**B. Calculate the input impedance, the output impedance, the output voltage and the bandwidth for the circuit shown in **Fig.2**. ( $C_{be1} = C_{be2} = 25$  pF,  $C_{bc1} = C_{bc2} = 10$  pF)**(8) Marks**

C. Compare between Field Effect Transistor and Bi-polar Junction Transistor?

**(4 marks)****Question No. 2 : (18) Marks**A. For the network of **Fig. 3**:**(8 marks)**

1. Determine the mathematical expression for the angle by which  $V_o$  leads  $V_i$ .
2. Determine the phase angle at  $f=100$  Hz, 1 kHz, 2 kHz, 5 kHz, and 10 kHz, and plot the resulting curve for the frequency range of 100 Hz to 10 kHz.
3. Determine the break frequency.
4. Sketch the frequency response of  $\theta$  for the same frequency spectrum of part (2) and compare results.

B. Using proofs, explain the advantages of the feedback?

**(5 marks)**C. By using proofs, explain the effect of the feedback on closed loop voltage gain, input impedance and output impedance for transconductance amplifier? **(5) Mark****Question No.3 : (18) Marks**A. Fig.4 shows a feedback circuit of the shunt-series type. Find  $I_{out}/I_{in}$ ,  $R_{in}$ , and  $R_{out}$ . Assume the transistor to have  $\beta=100$ . **(6 marks)**B. Consider an amplifier having a midband gain  $A_M$  and low-frequency response characterized by a pole  $s=-\omega_L$  and zero  $s=0$ . Let the amplifier

Use only black or blue pens or pencil in your answer

Do not make any mark in your booklet

Answer only the required questions (Extra answers will not be considered)

page No. (1 /4)

be connected in a negative-feedback loop with a feedback factor  $\beta$ . Find an expression for the midband gain and the lower 3-dB frequency of the closed-loop amplifier. By what factor have both changed?

(6 marks)

C. For the series-series feedback in Fig.5. If  $\mu=10^5$ ,  $R_{id}=10k\Omega$ ,  $r_o=100\Omega$ ,  $R_1=100\Omega$ ,  $R_2=10K\Omega$ ,  $R_L=1K\Omega$  and  $r=100\Omega$ . Find  $R_{if}$ ,  $R_{of}$ ,  $R_{in}$ ,  $R_{out}$ .

(6 marks)

Question No.4: (18) Marks

A. A filter has a transfer function  $T(s)=\frac{1}{(s+1)(s^2+s+1)}$ . Show that

$|T|=\sqrt{1+\omega^6}$  and find an expression for its phase response  $\phi(\omega)$ . Then calculate the values of  $|T|$  and  $\phi$  for  $\omega=0.1, 1, 10$  rad. Then find the output corresponding to the following input  $v_i=2\sin 0.1t$ . (9 marks)

B. An element ladder network has a minimum number of elements to realize a given  $Z(s)$ . two resistor have the value of A ohm and two capacitors A Farads. What are the possible forms of the driving point impedances  $Z(s)$ ? (9 marks)

Question No.5: (18) Marks

A. Sketch  $|T|$  for a seventh-order low pass Chebychev filter with  $w_p=1$  rad/second  $A_{max}=1dB$ . Determine the values of  $w$  at which  $|T|=1$  and the values of  $w$  at which  $|T|=\frac{1}{\sqrt{1+\epsilon^2}}$ . Indicate these values on your sketch. Determine  $|T|=1$  at  $w=2$  rad/sec, and indicate this point on your sketch. (6 marks)

B. Design a first order op-amp RC high pass filter having 3-dB frequency of 100Hz, a high frequency gain magnitude of unity, and a high input resistance of 100K $\Omega$ . (6 marks)

C. Synthesis the following driving point function  $s$  using first foster, first and second Cauer forms (6 marks)

$$Y(s)=\frac{3s(s^2+2)(s^2+5)(s^2+9)}{(s^2+1)(s^2+4)(s^2+7)}$$

Use only black or blue pens or pencil in your answer

Do not make any mark in your booklet

Answer only the required questions (Extra answers will not be considered)

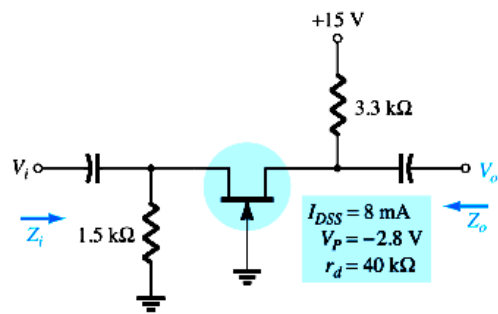


Fig.1

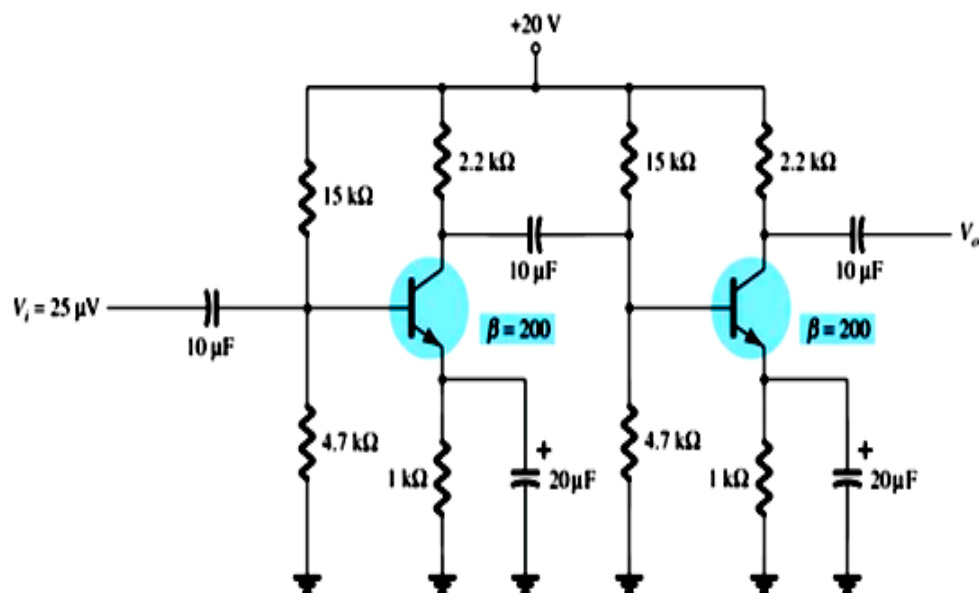


Fig.2

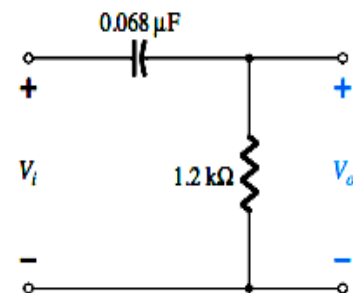


Fig.3

Use only black or blue pens or pencil in your answer  
 Do not make any mark in your booklet  
 Answer only the required questions (Extra answers will not be considered)  
 page No. (4 /4)

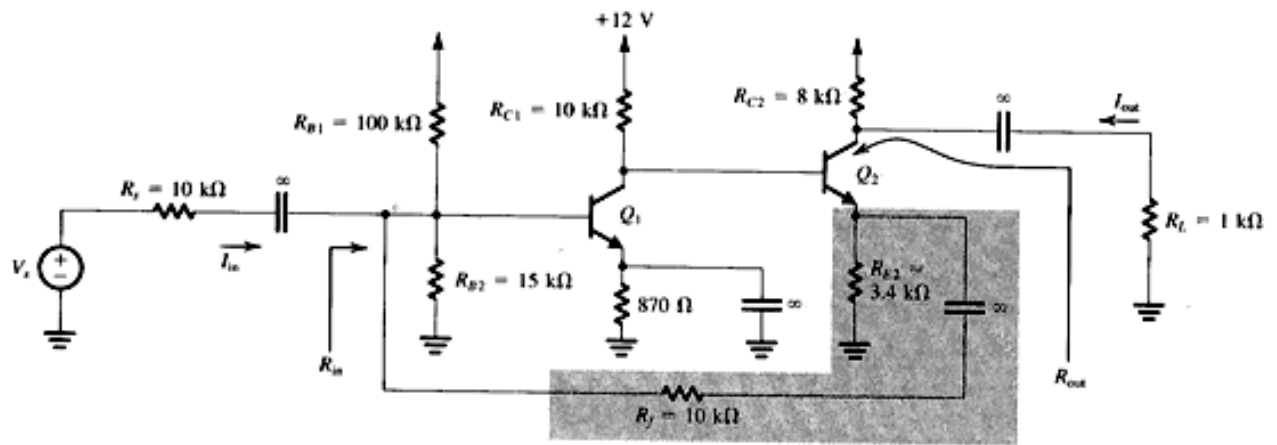


Fig.4

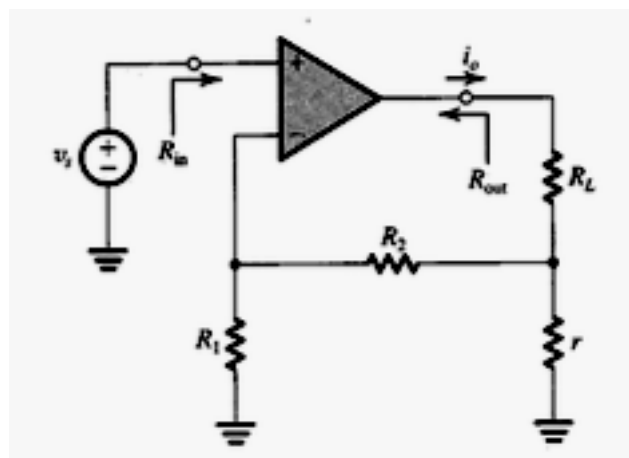


Fig.5

The end of questions

Good luck

Dr / Hossam Kasem (Coordinator of the Course)

Use only black or blue pens or pencil in your answer

Do not make any mark in your booklet

Answer only the required questions (Extra answers will not be considered)

page No. (4 /4)